

Gabriel Butterick

Parts 1&2:

Code

```
# Loading work.behavioralDecoder

# En A0 A1 | O0 O1 O2 O3 | Expected Output

# 0 0 0 | 0 0 0 0 | All false
# 0 1 0 | 0 0 0 0 | All false
# 0 0 1 | 0 0 0 0 | All false
# 0 1 1 | 0 0 0 0 | All false
# 1 0 0 | 1 0 0 0 | O0 Only
# 1 1 0 | 0 1 0 0 | O1 Only
# 1 0 1 | 0 0 1 0 | O2 Only
# 1 1 1 | 0 0 0 1 | O3 Only

# vsim

# Start time: 03:56:52 on Sep 25,2015

# Loading work.testFullAdder

# Loading work.behavioralFullAdder

# A B Ci | COut Sum | Expected Output

# 0 0 0 | 0 0 | Both False
# 0 1 0 | 0 1 | Sum True
# 1 0 0 | 0 1 | Sum True
# 1 1 0 | 1 0 | COut True
# 0 0 1 | 0 1 | Sum True
# 0 1 1 | 1 0 | COut True
# 1 0 1 | 1 0 | COut True
```

1 1 1 | 1 1 | Both True

vsim

Start time: 03:56:55 on Sep 25,2015

Loading work.testMultiplexer

Loading work.behavioralMultiplexer

a1 a0 | in0 in1 in2 in3 | out | Expected Output

0 0 | 0 0 0 0 | 0 0

0 0 | 0 0 0 1 | 0 0

0 0 | 0 0 1 0 | 0 0

0 0 | 0 0 1 1 | 0 0

0 0 | 0 1 0 0 | 0 0

0 0 | 0 1 0 1 | 0 0

0 0 | 0 1 1 0 | 0 0

0 0 | 0 1 1 1 | 0 0

0 0 | 1 0 0 0 | 1 0

0 0 | 1 0 0 1 | 1 0

0 0 | 1 0 1 0 | 1 0

0 0 | 1 0 1 1 | 1 0

0 0 | 1 1 0 0 | 1 0

0 0 | 1 1 0 1 | 1 0

0 0 | 1 1 1 0 | 1 0

0 0 | 1 1 1 1 | 1 0

0 1 | 0 0 0 0 | 0 1


0 1 | 0 0 0 1 | 0 1

0 1 | 0 0 1 0 | 1 1

# 0 1 0 0 1 1 1	1
# 0 1 0 1 0 0 0	1
# 0 1 0 1 0 1 0	1
# 0 1 0 1 1 0 1	1
# 0 1 0 1 1 1 1	1
# 0 1 1 0 0 0 0	1
# 0 1 1 0 0 1 0	1
# 0 1 1 0 1 0 1	1
# 0 1 1 0 1 1 1	1
# 0 1 1 1 0 0 0	1
# 0 1 1 1 0 1 0	1
# 0 1 1 1 1 0 1	1
# 0 1 1 1 1 1 1	1
# 1 0 0 0 0 0 0	2
# 1 0 0 0 0 1 0	2
# 1 0 0 0 1 0 0	2
# 1 0 0 0 1 1 0	2
# 1 0 0 1 0 0 1	2
# 1 0 0 1 0 1 1	2
# 1 0 0 1 1 0 1	2
# 1 0 0 1 1 1 1	2
# 1 0 1 0 0 0 0	2
# 1 0 1 0 0 1 0	2
# 1 0 1 0 1 0 0	2
# 1 0 1 0 1 1 0	2

# 1 0 1 1 0 0 1	2
# 1 0 1 1 0 1 1	2
# 1 0 1 1 1 0 1	2
# 1 0 1 1 1 1 1	2
# 1 1 0 0 0 0 0	3
# 1 1 0 0 0 1 1	3
# 1 1 0 0 1 0 0	3
# 1 1 0 0 1 1 1	3
# 1 1 0 1 0 0 0	3
# 1 1 0 1 0 1 1	3
# 1 1 0 1 1 0 0	3
# 1 1 0 1 1 1 1	3
# 1 1 1 0 0 0 0	3
# 1 1 1 0 0 1 1	3
# 1 1 1 0 1 0 0	3
# 1 1 1 0 1 1 1	3
# 1 1 1 1 0 0 0	3
# 1 1 1 1 0 1 1	3
# 1 1 1 1 1 0 0	3
# 1 1 1 1 1 1 1	3

Waveform

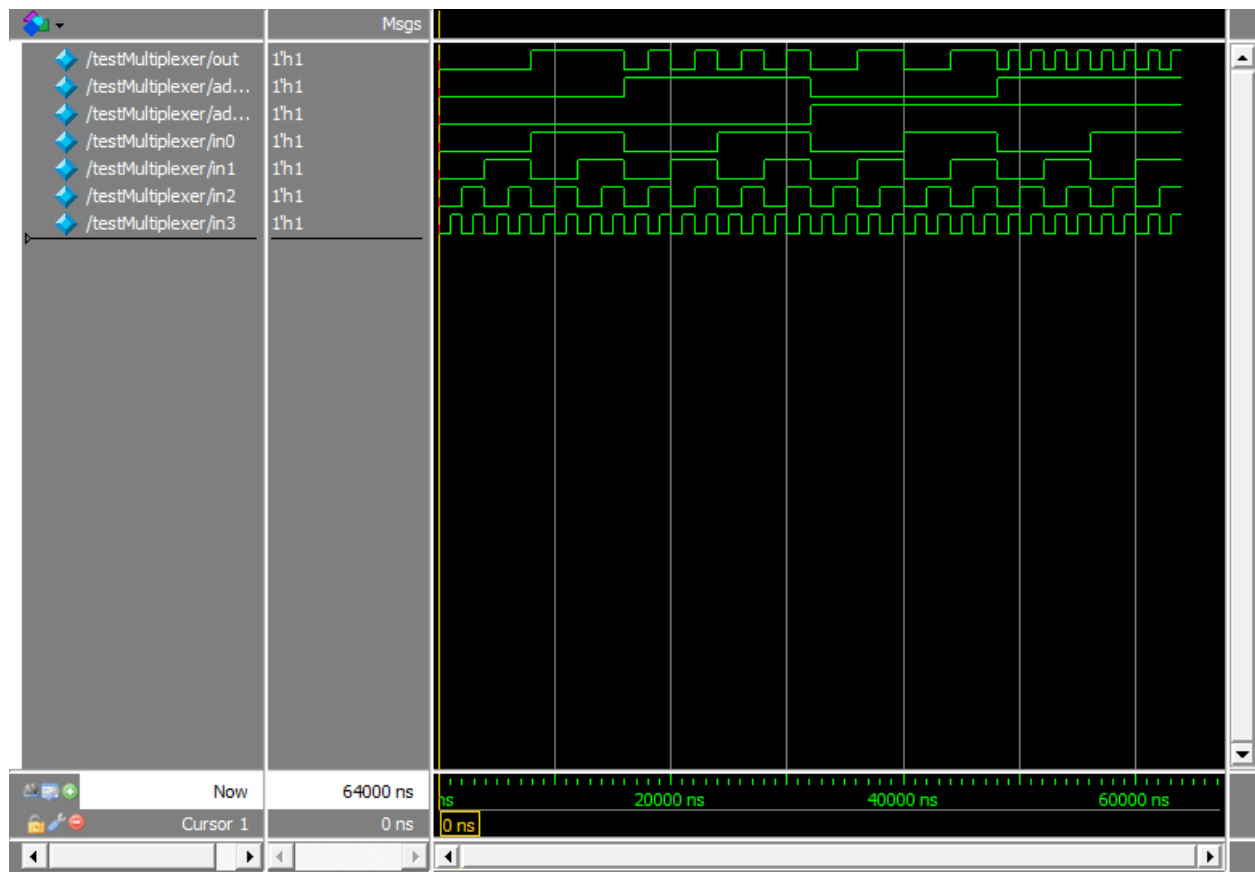

Parts 2&3

Code

Loading work.structuralDecoder

En A0 A1 | O0 O1 O2 O3 | Expected Output

0 0 0 | 0 0 0 0 | All false

0 1 0 | 0 0 0 0 | All false

0 0 1 | 0 0 0 0 | All false

0 1 1 | 0 0 0 0 | All false

1 0 0 | 1 0 0 0 | O0 Only

1 1 0 | 0 1 0 0 | O1 Only

1 0 1 | 0 0 1 0 | O2 Only

1 1 1 | 0 0 0 1 | O3 Only

vsim

Start time: 03:43:59 on Sep 25,2015

Loading work.testFullAdder

Loading work.structuralFullAdder

A B Ci | COut Sum | Expected Output

0 0 0 | 0 0 | Both False

0 1 0 | 0 1 | Sum True

1 0 0 | 0 1 | Sum True

1 1 0 | 1 0 | COut True

0 0 1 | 0 1 | Sum True

0 1 1 | 1 0 | COut True

1 0 1 | 1 0 | COut True

1 1 1 | 1 1 | Both True

vsim

Start time: 03:44:03 on Sep 25,2015

Loading work.testMultiplexer

Loading work.structuralMultiplexer

a1 a0 | in0 in1 in2 in3 | out | Expected Output

0 0 | 0 0 0 0 | 0 0

0 0 | 0 0 0 1 | 0 0

0 0 | 0 0 1 0 | 0 0

0 0 | 0 0 1 1 | 0 0

# 0 0 0 1 0 0 0	0
# 0 0 0 1 0 1 0	0
# 0 0 0 1 1 0 0	0
# 0 0 0 1 1 1 0	0
# 0 0 1 0 0 0 0	0
# 0 0 1 0 0 1 0	0
# 0 0 1 0 1 0 0	0
# 0 0 1 0 1 1 0	0
# 0 0 1 1 0 0 0	0
# 0 0 1 1 0 1 0	0
# 0 0 1 1 1 0 0	0
# 0 0 1 1 1 1 0	0
# 0 1 0 0 0 0 0	1
# 0 1 0 0 0 1 0	1
# 0 1 0 0 1 0 0	1
# 0 1 0 0 1 1 0	1
# 0 1 0 1 0 0 0	1
# 0 1 0 1 0 1 0	1
# 0 1 0 1 1 0 0	1
# 0 1 0 1 1 1 0	1
# 0 1 1 0 0 0 0	1
# 0 1 1 0 0 1 0	1
# 0 1 1 0 1 0 0	1
# 0 1 1 0 1 1 0	1
# 0 1 1 1 0 0 0	1

# 0 1 1 1 0 1 0	1
# 0 1 1 1 1 0 0	1
# 0 1 1 1 1 1 0	1
# 1 0 0 0 0 0 0	2
# 1 0 0 0 0 1 0	2
# 1 0 0 0 1 0 0	2
# 1 0 0 0 1 1 0	2
# 1 0 0 1 0 0 0	2
# 1 0 0 1 0 1 0	2
# 1 0 0 1 1 0 0	2
# 1 0 0 1 1 1 0	2
# 1 0 1 0 0 0 0	2
# 1 0 1 0 0 1 0	2
# 1 0 1 0 1 0 0	2
# 1 0 1 0 1 1 0	2
# 1 0 1 1 0 0 0	2
# 1 0 1 1 0 1 0	2
# 1 0 1 1 1 0 0	2
# 1 0 1 1 1 1 0	2
# 1 1 0 0 0 0 0	3
# 1 1 0 0 0 1 1	3
# 1 1 0 0 1 0 0	3
# 1 1 0 0 1 1 1	3
# 1 1 0 1 0 0 0	3
# 1 1 0 1 0 1 1	3

# 1 1 0 1 1 0 0	3
# 1 1 0 1 1 1 1	3
# 1 1 1 0 0 0 0	3
# 1 1 1 0 0 1 1	3
# 1 1 1 0 1 0 0	3
# 1 1 1 0 1 1 1	3
# 1 1 1 1 0 0 0	3
# 1 1 1 1 0 1 1	3
# 1 1 1 1 1 0 0	3
# 1 1 1 1 1 1 1	3

Waveform

